

Full Wave Rectifier

Full Wave Rectifier: Full wave rectifier using two diode and centre tapped transformer. When a is positive with respect to b diode D1 conducts for π radians. In the next half cycle b is positive with respect to a and therefore diode D2 conducts. The output voltage is shown as V_O . The waveform for output current i_o is similar to V_O waveform. When a is positive with respect to b, diode D2 is subjected to a reverse voltage of $2V_S$. In the next half cycle, diode D1 is a reverse voltage of $2V_S$. Thus, for diodes D1 and D2, peak inverse voltage is $2V_m$. So that for one cycle of source voltage, there are two pulses of output voltage.

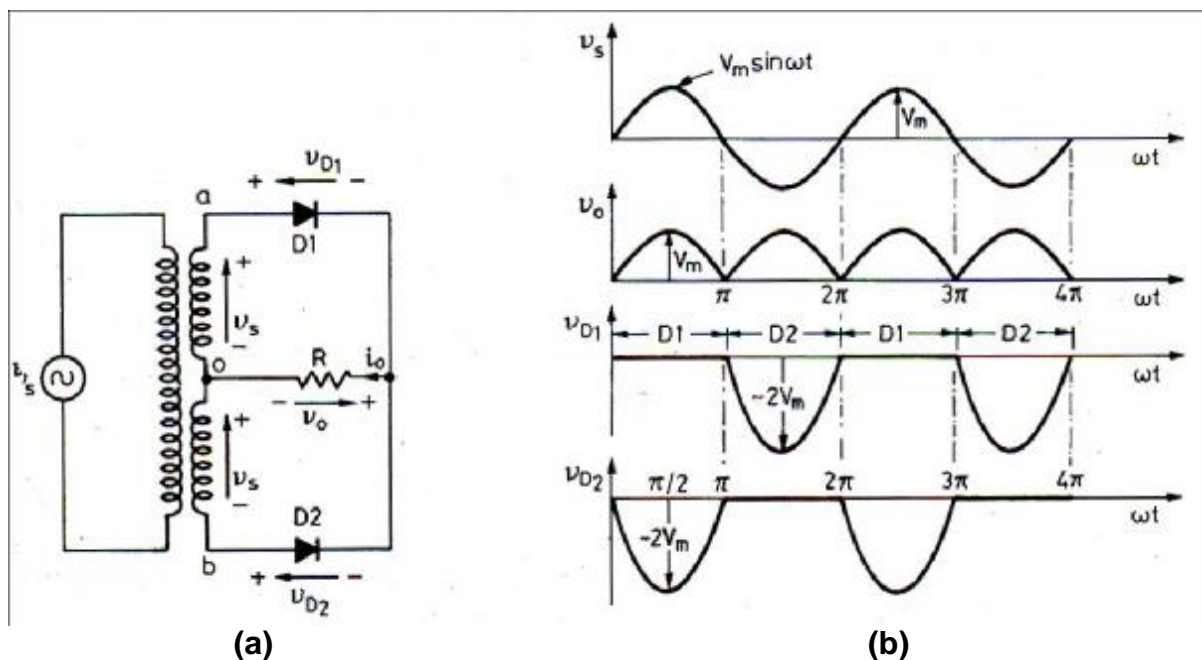


Fig. (a) Full Wave (Mid Point) Rectifier (b) Waveform of Full Wave Rectifier

So full wave diode rectifier can also be called two pulse diode rectifiers.

Average output voltage .

$$V_0 = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi}$$

Average output current ,

$$V_{or} = \left[\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d(\omega t) \right]^{1/2}$$

Rms value of output voltage ,

$$V_o = V_m / \sqrt{2} = V_s$$

Rms value of load current,

$$I_o = V_s / R$$

$$\begin{aligned}\text{Power delivered to load} &= V_o \cdot I_o \\ &= I_o^2 \cdot R \\ &= V_s \cdot I_o\end{aligned}$$