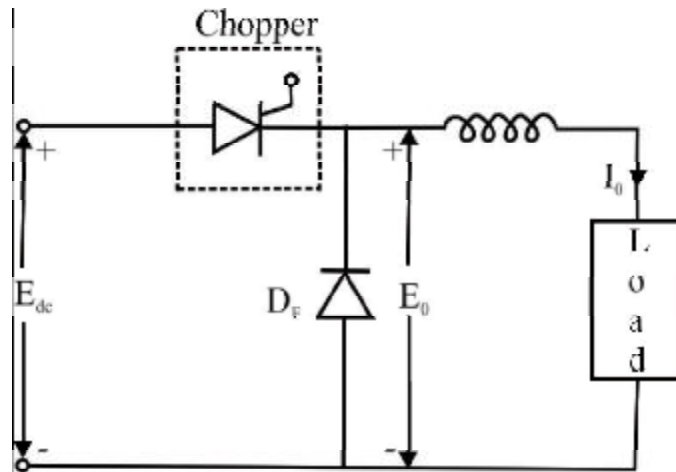


Step Down Chopper

Step Down Chopper:

A Chopper is simply an 'on-off' switch that either connects load to the supply or disconnects load from the supply and produces a chopped load voltage from a constant input supply. Figure shows the basic principle of Choppers.



Chopper Circuit

Figure 1

From the above figure it is clear that the SCR is triggered periodically and is kept conducting for a period T_{on} & is blocked for a period T_{off} . The chopped load voltage waveform is as shown in figure no. 2.

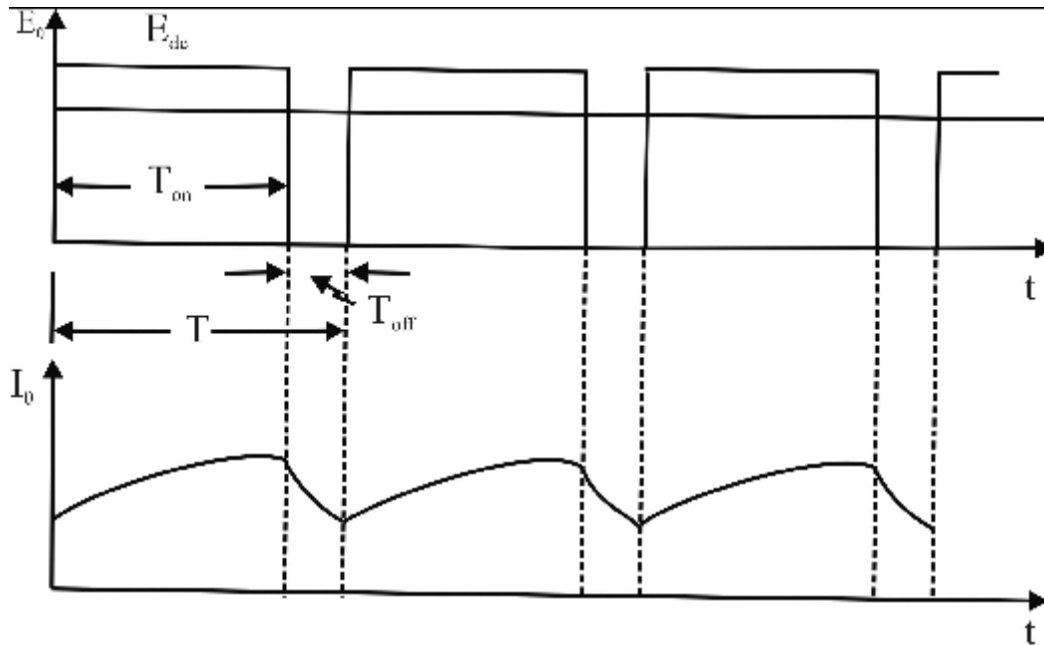


Figure 2

During the period T_{on} , when the chopper is on, the supply terminals are connected to the load terminals. & during the period T_{off} , when the chopper is 'Off', the load current flows through the Freewheeling Diode D_F . As a result, load terminals are short circuited by D_F & voltage therefore becomes zero during T_{off} . In this manner, a chopped DC voltage is produced at the load terminals. The average load-voltage E_o is given by

$$E_o = E_{dc} (T_{on}/T_{on}+T_{off}) \text{ Where}$$

T_{on} = 'On' time of the chopper.

T_{off} = 'Off' time of the chopper.

$T (T_{on}+T_{off})$ = Chopping period

If $\alpha = T_{on}/T$ be the duty cycle then above equation becomes,

$$E_o = E_{dc} \times (T_{on}/T)$$

$$E_o = E_{dc} \times \alpha$$

Thus the load voltage can be controlled by varying the duty cycle of the chopper.